## 一、填空题

- (1)  $1.2\Omega$ , 0.48W
- (2) -2A, 96W
- (3) (0.4 j1.2)V, (-2 + j6)V
- (4) (8-i6)VA,  $-36.9^{\circ}$
- (5)  $0.25 \mu F$ ,  $5 \cos(1000t + 20^{\circ}) A$
- (6)  $(1 e^{-10t})\varepsilon(t)V$ ,  $[0.1\delta(t) e^{-10t}\varepsilon(t)]A$

## 二、计算题

(1) 
$$U_{OC} = 0.6 \,\mathrm{V}, R_{eq} = 2\Omega;$$

$$U = -\frac{2}{15}V, I = \frac{11}{30}A$$

(2) 
$$A = \begin{bmatrix} \frac{3}{5} & \frac{3}{5}\Omega \\ \frac{4}{15}S & \frac{3}{5} \end{bmatrix}$$
,  $Z = \begin{bmatrix} \frac{9}{4} & \frac{3}{4} \\ \frac{15}{4} & \frac{9}{4} \end{bmatrix} \Omega$ 

(3) 
$$H(j\omega) = \frac{1}{1 - \omega^2 + j3\omega}$$
,  $u_2(t) = \frac{2}{3}\sqrt{10}\cos(2t - 116.6^\circ)$ V

(4) 
$$i_L(t) = (\frac{2}{3} - \frac{1}{6}e^{-3t})A, t \ge 0$$

(5) 
$$u_C(t) = (1 - \frac{15}{4}e^{-2t} + \frac{15}{4}e^{-3t})V, t \ge 0$$